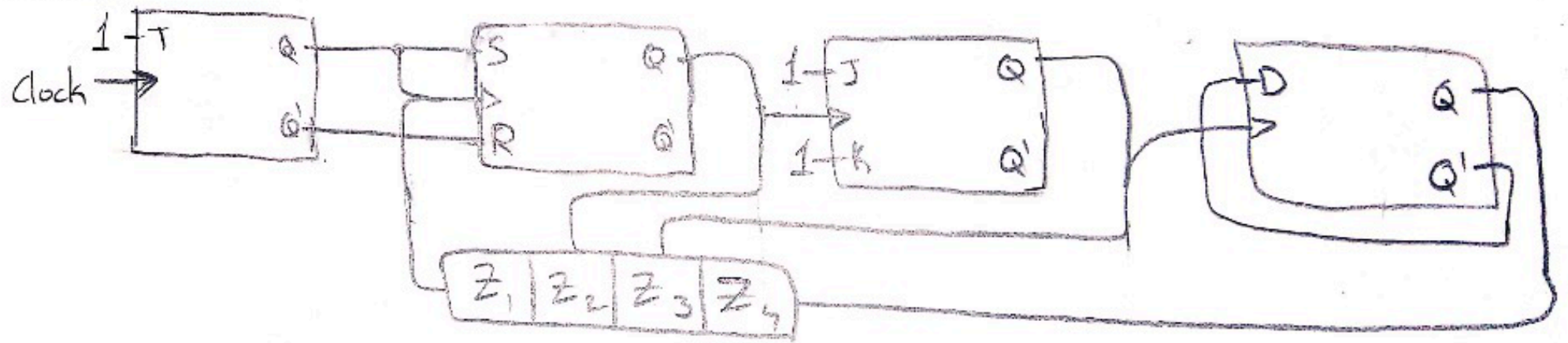



Soru 1



Soru 2

Sonraki Durum

Mevcut Durum	Sonraki Durum										z_1, z_2, z_3, z_4			
	F_1, F_2	L_1, L_2 0 0	L_1, L_2 0 1	L_1, L_2 1 0	L_1, L_2 1 1	L_1, L_2 0 0	L_1, L_2 0 1	L_1, L_2 1 0	L_1, L_2 1 1	L_1, L_2 0 0				
A)	0 0	0 0	0 1	1 1	1 0	0 0	0 1	1 1	1 0	0 0	0 0	1	0	0
B)	0 1	0 1	1 0	0 0	1 1	0 1	1 0	0 0	1 1	0 0	0 0	0	0	0
C)	1 0	1 0	1 1	0 1	0 0	1 0	1 1	0 1	0 0	0 1	0	1	1	0
D)	1 1	1 1	0 0	1 0	0 1	1 1	0 0	1 0	0 1	1 0	1	0	0	0

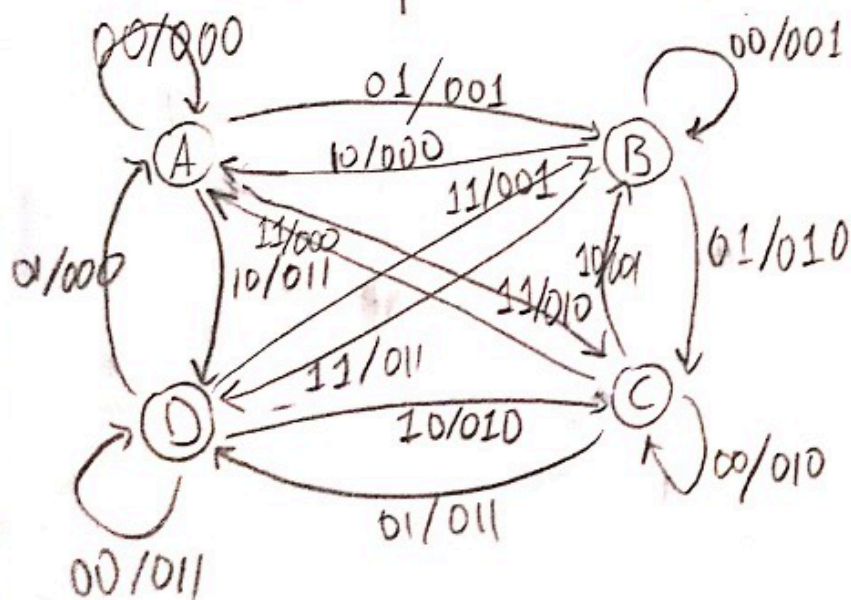

F_1, F_2	L_1, L_2 0 0	L_1, L_2 0 1	L_1, L_2 1 0	L_1, L_2 1 1
0 0	0	0	1	1
0 1	0	0	1	0
1 1	1	0	0	1
1 0	1	1	0	0

$$D_1 = F_1 F_2 L_1' + L_1 F_1' F_2' + L_1 L_2 F_1' + F_1 F_2 L_2'$$

F_1, F_2	L_1, L_2 0 0	L_1, L_2 0 1	L_1, L_2 1 0	L_1, L_2 1 1
0 0	0	1	0	1
0 1	1	0	1	0
1 1	1	0	1	0
1 0	0	1	0	1

$$D_2 = F_2 L_1' L_2' + F_2' L_1' L_2 + L_1 L_2 F_2 + L_1 L_2 F_2'$$

F_1, F_2	0	1
0	0	0
1	0	1

$z_1 = F_1 F_2$

F_1, F_2	0	1
0	0	0
1	1	0

$z_2 = F_1 F_2$

F_1, F_2	0	1
0	1	0
1	1	0

$z_3 = F_2'$

F_1, F_2	0	1
0	0	0
1	0	0

$z_4 = 0$